
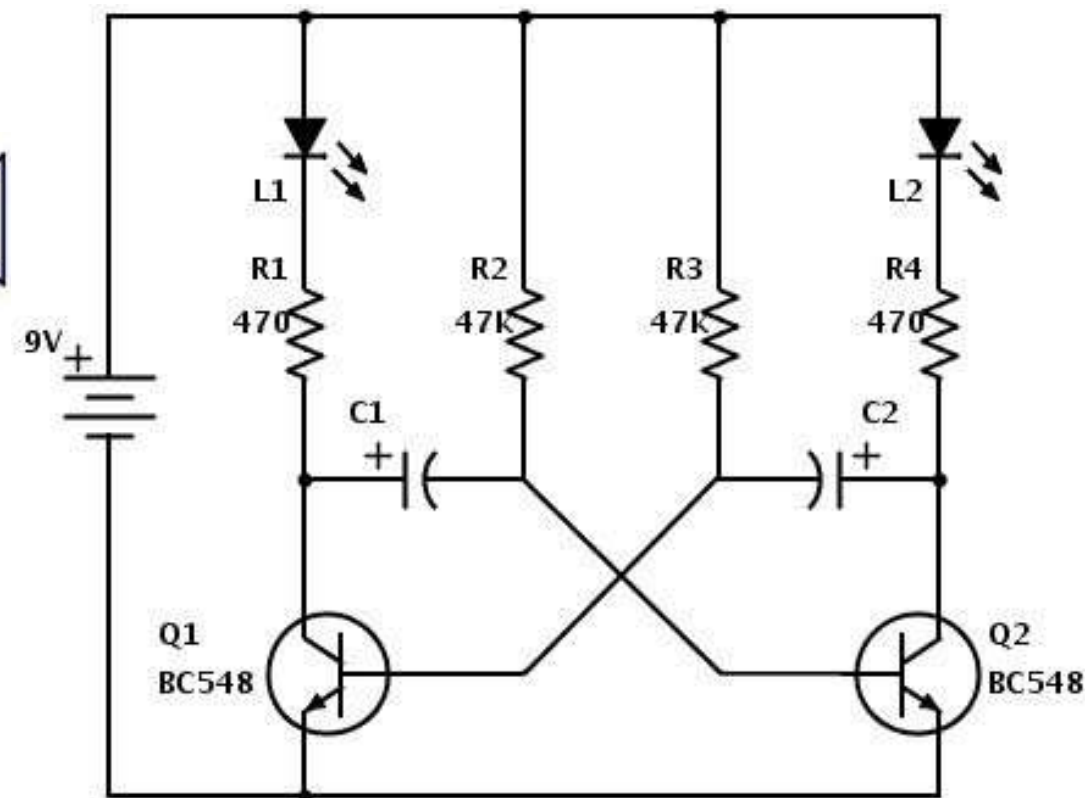


Concluding Unit 1

Electronics symbol



- An **electronic symbol** is a [pictogram](#) used to represent various [electrical](#) and [electronic](#) devices or functions, such as [wires](#), [batteries](#), [resistors](#), and [transistors](#), in a [schematic diagram](#) of an electrical or [electronic circuit](#). These symbols are largely standardized internationally today, but may vary from country to country, or engineering discipline, based on traditional conventions.

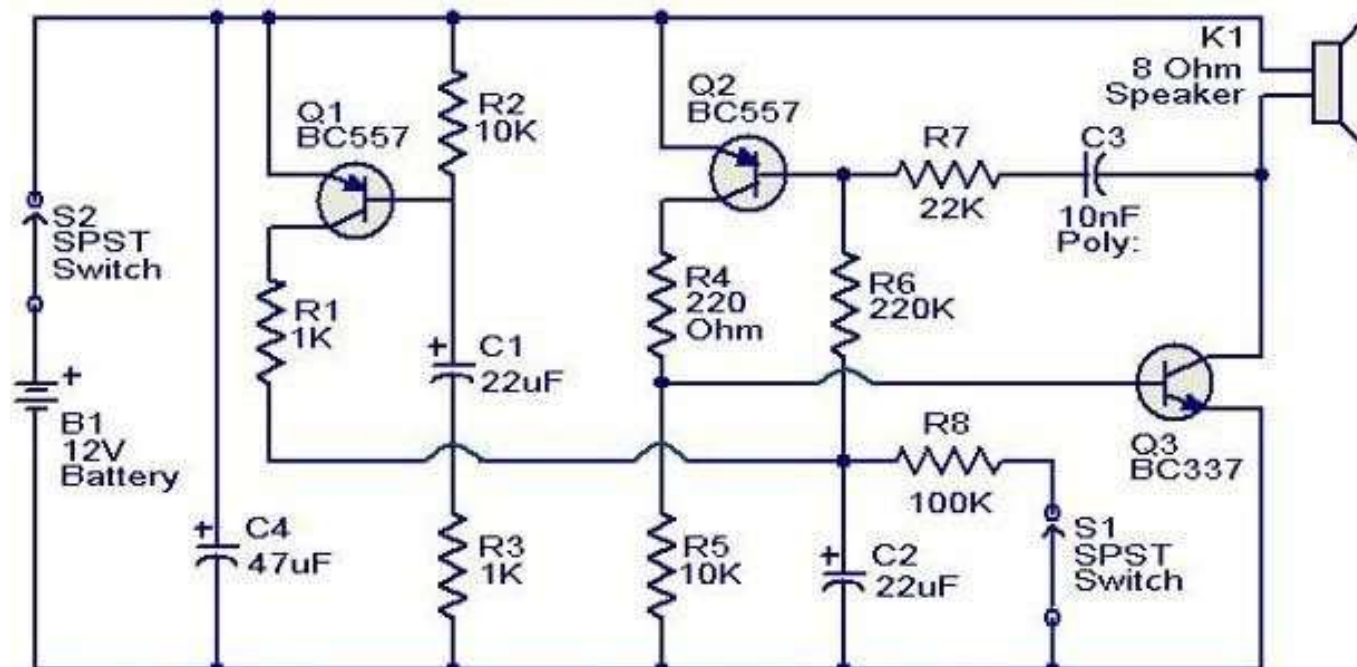

Source

An electrical source is a **device that is capable of converting non-electrical energy into electrical energy**

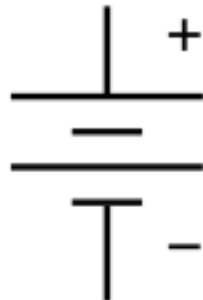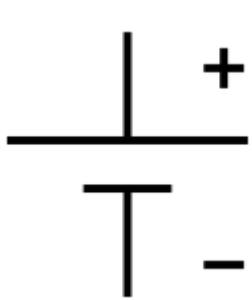An example of this is a battery that can convert chemical energy into electrical energy.



Resistor

A **resistor** is a passive two-terminal electrical component that implements electrical resistance as a circuit element.




LED

A **light-emitting diode (LED)** is a semiconductor light source that emits light when current flows through it.




Capacitor

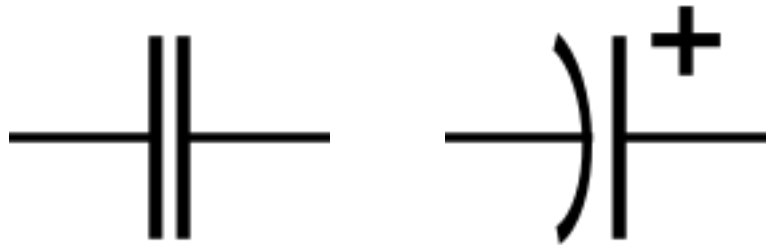A **capacitor** is a device that stores electrical energy in an electric field. It is a passive electronic component with two terminals.




Transistor

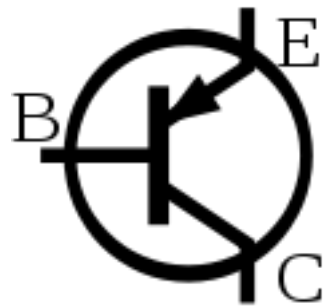
A **transistor** is a semiconductor device used to amplify or switch electrical signals and power.



PNP

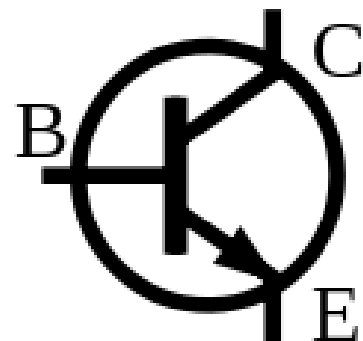


NPN

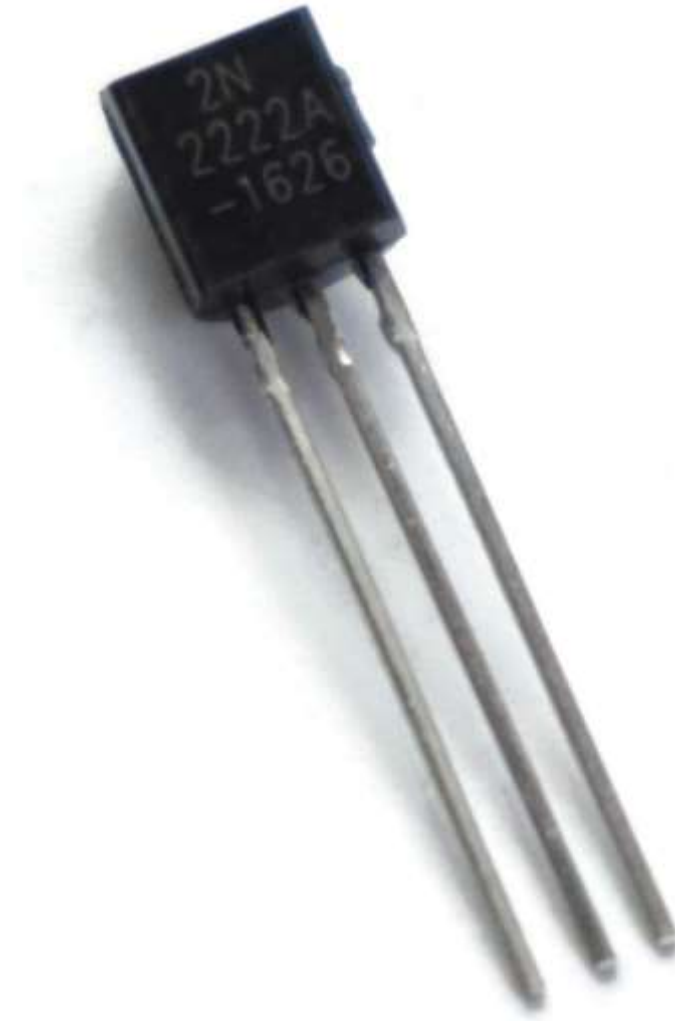


Switch

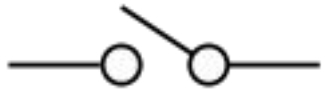A switch is a **small control for an electrical device which you use to turn the device on or off.**



Single-pole

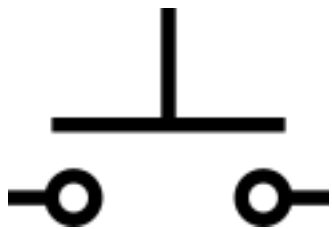

Pushbutton




Diode


Diode, an electrical component that allows the flow of current in only one direction.



Trace

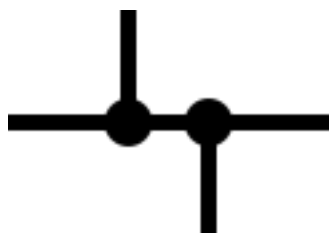

Trace junction

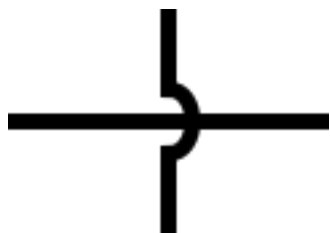

Trace crossing

Buzzer

A buzzer or beeper is **an audio signaling device**, which may be mechanical, electromechanical, or piezoelectric (piezo for short).





Polarity to the component

- Polarity is also important **for determining the direction of current flow.**
- A polarized component, a part with polarity, **can only be connected in a circuit in one direction.**

Eg.batteries, integrated circuits, transistors, voltage regulators, electrolytic capacitors, and diodes

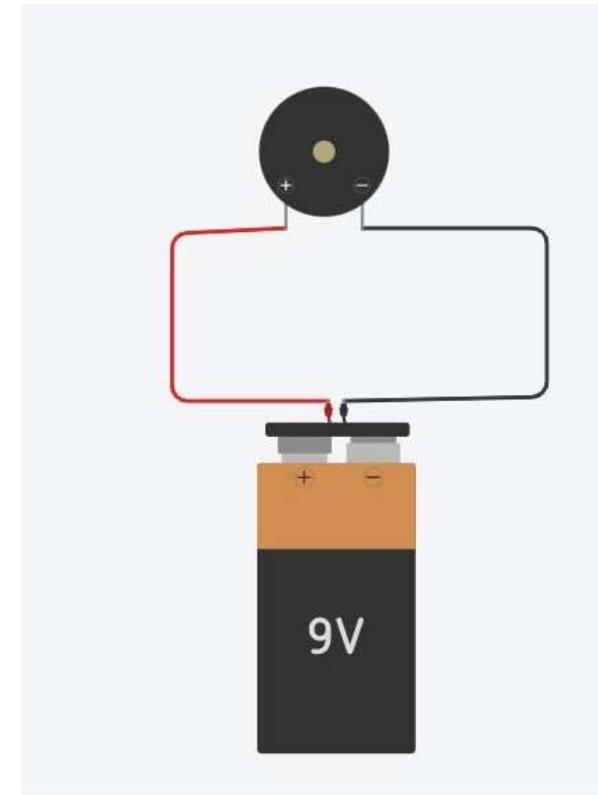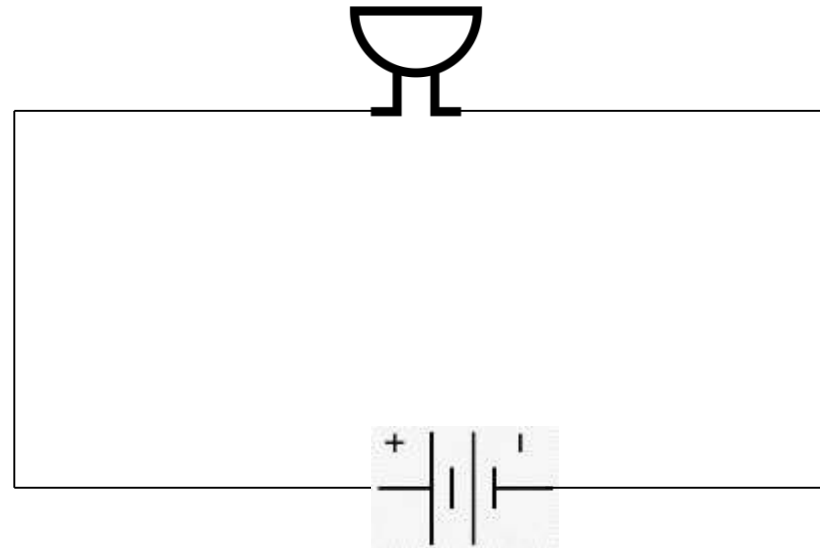
- Non polarized component -A non-polarized component -- **a part without polarity** -- can be connected in any direction and still function the way it's supposed to function
- E.g. Resistor



Activity

- Draw circuit
- Write down used component with quantity

Circuit 1

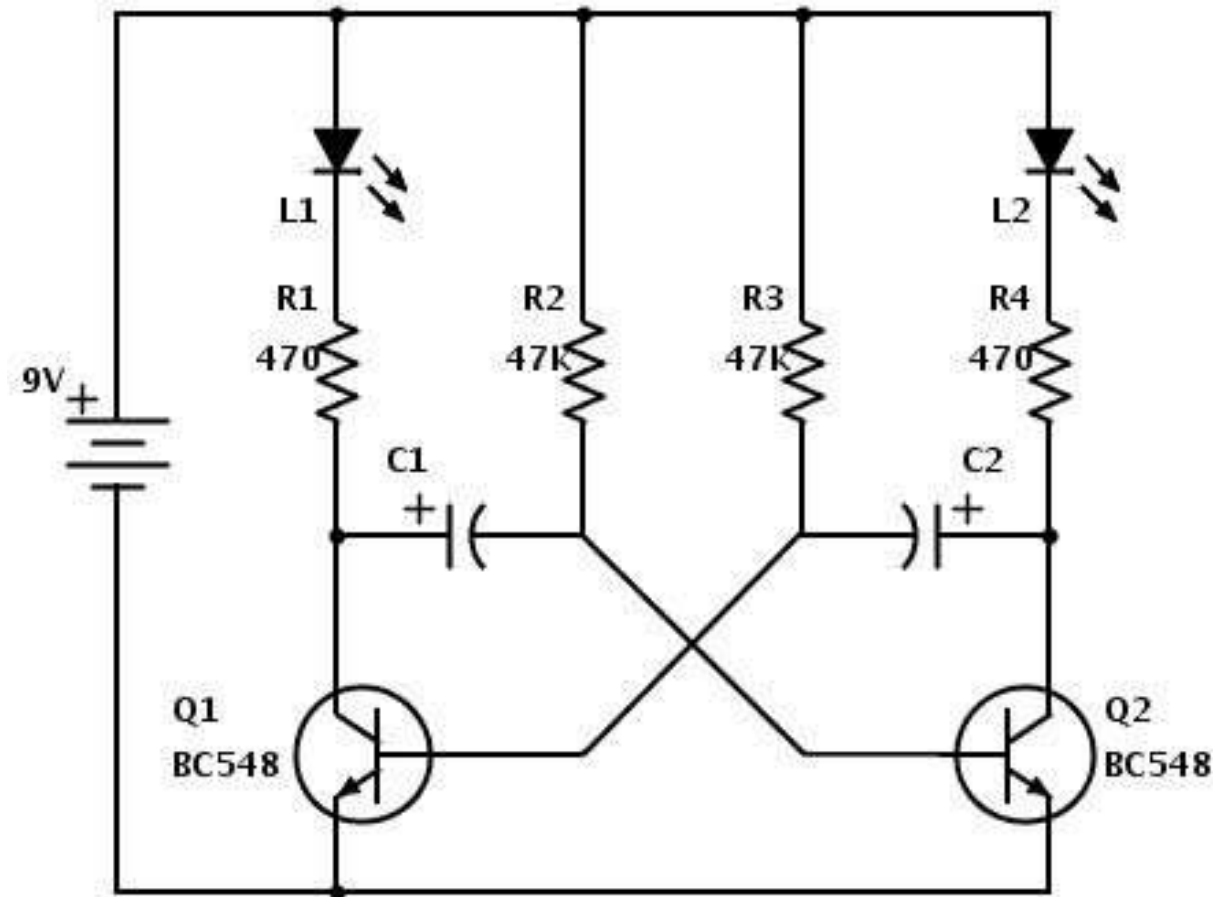

Arduino programming Command

- **Void setup-**To put your setup code here, to run once
- **Void loop-** put your main code here, to run repeatedly
- **pin Mode(pin,Mode)-**The Arduino pin number to set the mode of.
mode: INPUT, OUTPUT,
- **Delay()-**to provide time
- **HIGH-**On condition
- **LOW-**low condition
- **digitalWrite()-**write data to digital pin from Arduino

Micro-controller –ATMEGA 328



Arduino

Code

```
void setup()
{
  pinMode(13, OUTPUT);
}
void loop()
{
  digitalWrite(13, HIGH);
  delay(1000); // Wait for 1000 millisecond(s)
  digitalWrite(13, LOW);
  delay(1000); // Wait for 1000 millisecond(s)
}
```

Seven Segment display

- A seven-segment display is a form of electronic display device for displaying decimal numerals

